

Table of Contents

Experiment no.	Experiment name	Remarks
1.	Performance analysis of half-wave rectifier with resistive & inductive load	
2.	Experimental investigation of half-wave-controlled rectifier with resistive & inductive load	
3.	Experimental study of single phase-controlled rectifier with resistive, inductive, & resistive -inductive load	
4.	Experimental investigation of half wave and full wave AC voltage controller	
5.	Experimental analysis of 555 timer-based boost converter	