

*Heaven's light is our guide.*

# Rajshahi University of Engineering and Technology



Department of Electrical & Electronic Engineering

Course no.

EEE3212

Course title:

Power Sytem I Sessional

Experiment no.

08

Experiment name:

Transient response analysis of a series RL circuit to imitate the terminal fault of an unloaded alternator

Date of experiment:

December 11,2022

Date of submission:

December 18, 2022

<b>Submitted to:</b>	<b>Submitted by:</b>
<b>Md. Nuhi-Alamin</b>	<b>Ashraf Al- Khaliq</b>
<b>Lecturer</b>	<b>Roll: 1801171</b>
Dept. of Electrical & Electronic Engineering, Rajshahi University of Engineering and Technology.	<b>Session: 2018-2019</b> Dept. of Electrical & Electronic Engineering, Rajshahi University of Engineering and Technology.